
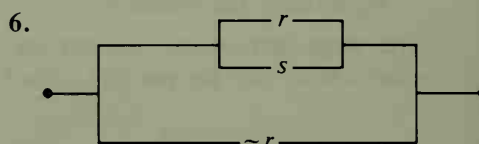
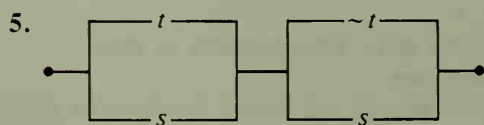
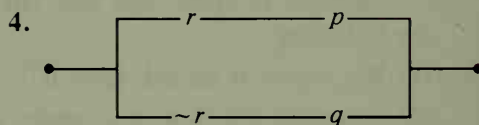
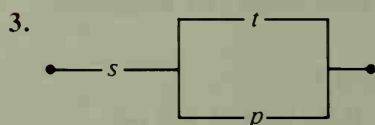


| $p$ | $q$ | $\sim q$ | $p \wedge q$ | $p \wedge \sim q$ | $(p \wedge q) \vee (p \wedge \sim q)$ |
|-----|-----|----------|--------------|-------------------|---------------------------------------|
| T   | T   | F        | T            | F                 | T                                     |
| T   | F   | T        | F            | T                 | T                                     |
| F   | T   | F        | F            | F                 | F                                     |
| F   | F   | T        | F            | F                 | F                                     |

Notice that the first and last columns of the truth table are identical. This means that the complicated circuit shown can be replaced by a simpler circuit that contains just switch  $p$ ! In other words, logic can be used to replace a complex electrical circuit by a simpler one.
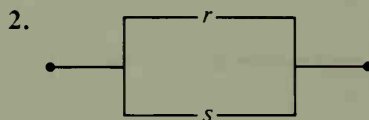
## Exercises

Symbolize each circuit using  $\wedge$ ,  $\vee$ ,  $\sim$ , and letters given for the switches in each diagram.



- Draw a diagram for the circuit  $p \wedge \sim p$ ; also for the circuit  $p \vee \sim p$ . Electricity can always pass through one of these circuits and can never pass through the other. Which is which?
- According to the commutative rule,  $p \wedge q \equiv q \wedge p$ . This means that the circuit  $p \wedge q$  does the same thing as the circuit  $q \wedge p$ . Make a diagram of each circuit.
- According to the associative rule,  $(p \vee q) \vee r \equiv p \vee (q \vee r)$ . Draw diagrams for each circuit.
- The distributive rule says that  $p \wedge (q \vee r) \equiv (p \wedge q) \vee (p \wedge r)$ . Draw diagrams for each circuit.
- Make both a diagram and a truth table for the circuit  $(p \vee q) \vee \sim q$ . Notice that the last column of your table is always T so that current always flows. This means that all of the switches could be eliminated.
- Make both a diagram and a truth table for the circuit  $(p \vee q) \wedge (p \vee \sim q)$ . Describe a simpler circuit equivalent to this circuit.