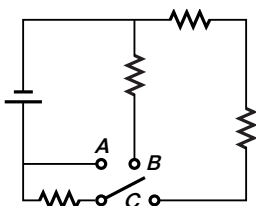



## SCHEMATIC DIAGRAMS AND CIRCUITS
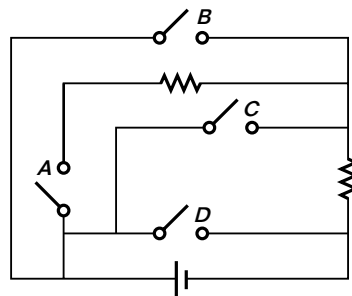
### Review Questions

- Why are schematic diagrams useful?
- Draw a circuit diagram for a circuit containing three  $5.0\ \Omega$  resistors, a  $6.0\ \text{V}$  battery, and a switch.
- The switch in the circuit shown at right can be set to connect to points *A*, *B*, or *C*. Which of these connections will provide a complete circuit?
- If the batteries in a cassette recorder provide a terminal voltage of  $12.0\ \text{V}$ , what is the potential difference across the entire recorder?
- In a case in which the internal resistance of a battery is significant, which is greater?
  - the terminal voltage
  - the emf of the battery



- Which of the switches in the circuit below will complete a circuit when closed? Which will cause a short circuit?



## RESISTORS IN SERIES OR IN PARALLEL

### Review Questions

- If four resistors in a circuit are connected in series, which of the following is the same for the resistors in the circuit?
  - potential difference across the resistors
  - current in the resistors
- If four resistors in a circuit are in parallel, which of the following is the same for the resistors in the circuit?
  - potential difference across the resistors
  - current in the resistors

### Conceptual Questions

- Do charges move from a source of potential difference into a load or through both the source and the load?
- Assuming that you want to create a circuit that has current in it, why should there be no openings in the circuit?
- Suppose a  $9\ \text{V}$  battery is connected across a light bulb. In what form is the electrical energy supplied by the battery dissipated by the light bulb?
- Why is it dangerous to use an electrical appliance when you are in the bathtub?

### Conceptual Questions

- A short circuit is a circuit containing a path of very low resistance in parallel with some other part of the circuit. Discuss the effect of a short circuit on the current within the portion of the circuit that has very low resistance.
- Fuses protect electrical devices by opening a circuit if the current in the circuit is too high. Would a fuse work successfully if it were connected in parallel with the device that it is supposed to protect?