

Substitute the equivalent resistance value into the equation for current.

$$I = \frac{\Delta V}{R_{eq}} = \frac{9.0 \text{ V}}{18.0 \Omega}$$

$$I = 0.50 \text{ A}$$

**4. EVALUATE** For resistors connected in series, the equivalent resistance should be greater than the largest resistance in the circuit.

$$18.0 \Omega > 7.0 \Omega$$

## PRACTICE A

### Resistors in Series

1. A 12.0 V storage battery is connected to three resistors, 6.75  $\Omega$ , 15.3  $\Omega$ , and 21.6  $\Omega$ , respectively. The resistors are joined in series.
  - a. Calculate the equivalent resistance.
  - b. What is the current in the circuit?
2. A 4.0  $\Omega$  resistor, an 8.0  $\Omega$  resistor, and a 12.0  $\Omega$  resistor are connected in series with a 24.0 V battery.
  - a. Calculate the equivalent resistance.
  - b. Calculate the current in the circuit.
  - c. What is the current in each resistor?
3. Because the current in the equivalent resistor of Sample Problem A is 0.50 A, it must also be the current in each resistor of the original circuit. Find the potential difference across each resistor.
4. A series combination of two resistors, 7.25  $\Omega$  and 4.03  $\Omega$ , is connected to a 9.00 V battery.
  - a. Calculate the equivalent resistance of the circuit and the current.
  - b. What is the potential difference across each resistor?
5. A 7.0  $\Omega$  resistor is connected in series with another resistor and a 4.5 V battery. The current in the circuit is 0.60 A. Calculate the value of the unknown resistance.
6. Several light bulbs are connected in series across a 115 V source of emf.
  - a. What is the equivalent resistance if the current in the circuit is 1.70 A?
  - b. If each light bulb has a resistance of 1.50  $\Omega$ , how many light bulbs are in the circuit?