

Because the current in each bulb is equal to the total current, you can also use $\Delta V = IR$ to calculate the potential difference across each resistor.

$$\Delta V_1 = IR_1 \quad \text{and} \quad \Delta V_2 = IR_2$$


The method described above can be used to find the potential difference across resistors in a series circuit containing any number of resistors.

SAMPLE PROBLEM A

Resistors in Series

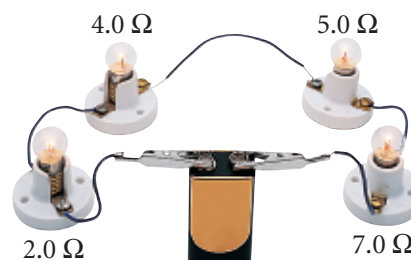PROBLEM

A 9.0 V battery is connected to four light bulbs, as shown at right. Find the equivalent resistance for the circuit and the current in the circuit.




SOLUTION

1. DEFINE

Given: $\Delta V = 9.0 \text{ V}$ $R_1 = 2.0 \text{ } \Omega$
 $R_2 = 4.0 \text{ } \Omega$ $R_3 = 5.0 \text{ } \Omega$
 $R_4 = 7.0 \text{ } \Omega$

Unknown: $R_{eq} = ?$ $I = ?$

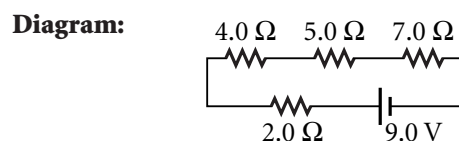

2. PLAN

Choose an equation or situation:

Because the resistors are connected end to end, they are in series. Thus, the equivalent resistance can be calculated with the equation for resistors in series.

$$R_{eq} = R_1 + R_2 + R_3 \dots$$

The following equation can be used to calculate the current.

$$\Delta V = IR_{eq}$$

Rearrange the equation to isolate the unknown:

No rearrangement is necessary to calculate R_{eq} , but $\Delta V = IR_{eq}$ must be rearranged to calculate current.

$$I = \frac{\Delta V}{R_{eq}}$$

3. CALCULATE

Substitute the values into the equation and solve:

$$R_{eq} = 2.0 \text{ } \Omega + 4.0 \text{ } \Omega + 5.0 \text{ } \Omega + 7.0 \text{ } \Omega$$

$$R_{eq} = 18.0 \text{ } \Omega$$

continued on
next page