

KEY IDEAS

Section 1 Schematic Diagrams and Circuits

- Schematic diagrams use standardized symbols to summarize the contents of electric circuits.
- A circuit is a set of electrical components connected so that they provide one or more complete paths for the movement of charges.
- Any device that transforms nonelectrical energy into electrical energy, such as a battery or a generator, is a source of emf.
- If the internal resistance of a battery is neglected, the emf can be considered equal to the terminal voltage, the potential difference across the source's two terminals.

Section 2 Resistors in Series or in Parallel

- Resistors in series have the same current.
- The equivalent resistance of a set of resistors connected in series is the sum of the individual resistances.
- The sum of currents in parallel resistors equals the total current.
- The equivalent resistance of a set of resistors connected in parallel is calculated using an inverse relationship.

Section 3 Complex Resistor Combinations

- Many complex circuits can be understood by isolating segments that are in series or in parallel and simplifying them to their equivalent resistances.

KEY TERMS

schematic diagram (p. 640)

electric circuit (p. 642)

series (p. 647)

parallel (p. 651)

PROBLEM SOLVING

See **Appendix D: Equations** for a summary of the equations introduced in this chapter. If you need more problem-solving practice, see **Appendix I: Additional Problems**.

Variable Symbols

Quantities	Units	Conversions
I current	A amperes	$= C/s$ $= \text{coulombs of charge per second}$
R resistance	Ω ohms	$= V/A$ $= \text{volts per ampere of current}$
ΔV potential difference	V volts	$= J/C$ $= \text{joules of energy per coulomb of charge}$

Diagram Symbols

Wire or conductor



Resistor or circuit load




Bulb or lamp



Plug



Battery/
direct-current
emf source

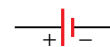

Switch



Capacitor

