

SAMPLE PROBLEM B

rms Current and emf

PROBLEM

A generator with a maximum output emf of 205 V is connected to a 115 Ω resistor. Calculate the rms potential difference. Find the rms current through the resistor. Find the maximum ac current in the circuit.


SOLUTION

1. DEFINE

Given: $\Delta V_{max} = 205 \text{ V}$ $R = 115 \Omega$

Unknown: $\Delta V_{rms} = ?$ $I_{rms} = ?$ $I_{max} = ?$

Diagram:

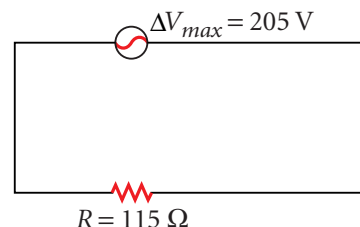

2. PLAN

Choose an equation or situation: Use the equation for the rms potential difference to find ΔV_{rms} .

$$\Delta V_{rms} = 0.707 \Delta V_{max}$$

Rearrange the definition for resistance to calculate I_{rms} .

$$I_{rms} = \frac{\Delta V_{rms}}{R}$$

Use the equation for rms current to find I_{max} .

$$I_{rms} = 0.707 I_{max}$$

Rearrange the equation to isolate the unknown:

Rearrange the equation relating rms current to maximum current so that maximum current is calculated.

$$I_{max} = \frac{I_{rms}}{0.707}$$



Because emf is measured in volts, maximum emf is frequently abbreviated as ΔV_{max} , and rms emf can be abbreviated as ΔV_{rms} .

3. CALCULATE

Substitute the values into the equation and solve:

$$\Delta V_{rms} = (0.707)(205 \text{ V}) = 145 \text{ V}$$

$$I_{rms} = \frac{145 \text{ V}}{115 \Omega} = 1.26 \text{ A}$$

$$I_{max} = \frac{1.26 \text{ A}}{0.707} = 1.78 \text{ A}$$

$$\begin{aligned} \Delta V_{rms} &= 145 \text{ V} \\ I_{rms} &= 1.26 \text{ A} \\ I_{max} &= 1.78 \text{ A} \end{aligned}$$

4. EVALUATE

The rms values for the emf and current are a little more than two-thirds the maximum values, as expected.