
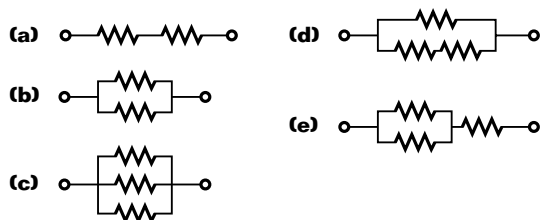


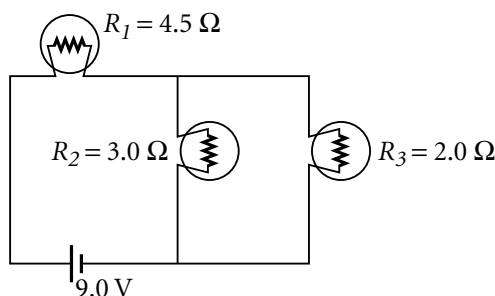35. The figures (a)–(e) below depict five resistance diagrams. Each individual resistance is $6.0\ \Omega$.
- Which resistance combination has the largest equivalent resistance?
 - Which resistance combination has the smallest equivalent resistance?
 - Which resistance combination has an equivalent resistance of $4.0\ \Omega$?
 - Which resistance combination has an equivalent resistance of $9.0\ \Omega$?




36. Three small lamps are connected to a $9.0\ \text{V}$ battery, as shown below.
- What is the equivalent resistance of this circuit?
 - What is the current in the battery?
 - What is the current in each bulb?
 - What is the potential difference across each bulb?



37. An $18.0\ \Omega$ resistor and a $6.0\ \Omega$ resistor are connected in series to an $18.0\ \text{V}$ battery. Find the current in and the potential difference across each resistor.
38. A $30.0\ \Omega$ resistor is connected in parallel to a $15.0\ \Omega$ resistor. These are joined in series to a $5.00\ \Omega$ resistor and a source with a potential difference of $30.0\ \text{V}$.
- Draw a schematic diagram for this circuit.
 - Calculate the equivalent resistance.
 - Calculate the current in each resistor.
 - Calculate the potential difference across each resistor.

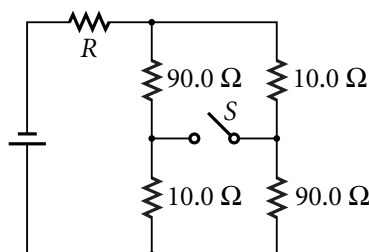39. A resistor with an unknown resistance is connected in parallel to a $12\ \Omega$ resistor. When both resistors are connected to an emf source of $12\ \text{V}$, the current in the unknown resistor is measured with an ammeter to be $3.0\ \text{A}$. What is the resistance of the unknown resistor?
40. The resistors described in item 37 are reconnected in parallel to the same $18.0\ \text{V}$ battery. Find the current in each resistor and the potential difference across each resistor.
41. The equivalent resistance for the circuit shown below drops to one-half its original value when the switch, S , is closed. Determine the value of R .



42. You can obtain only four $20.0\ \Omega$ resistors from the stockroom.
- How can you achieve a resistance of $50.0\ \Omega$ under these circumstances?
 - What can you do if you need a $5.0\ \Omega$ resistor?
43. Four resistors are connected to a battery with a terminal voltage of $12.0\ \text{V}$, as shown below. Determine the following:
- the equivalent resistance for the circuit
 - the current in the battery
 - the current in the $30.0\ \Omega$ resistor
 - the power dissipated by the $50.0\ \Omega$ resistor
 - the power dissipated by the $20.0\ \Omega$ resistor

(Hint: Remember that $P = \frac{(\Delta V)^2}{R} = I\Delta V$.)

